
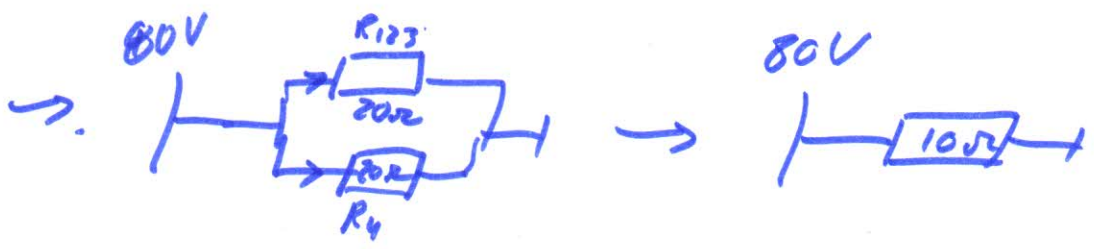
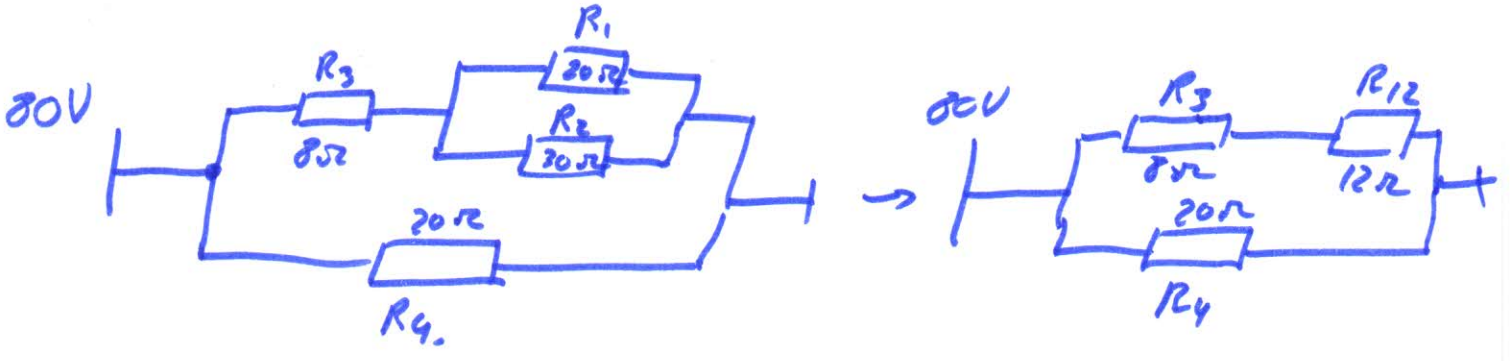


Problema clase.

27-1-2020

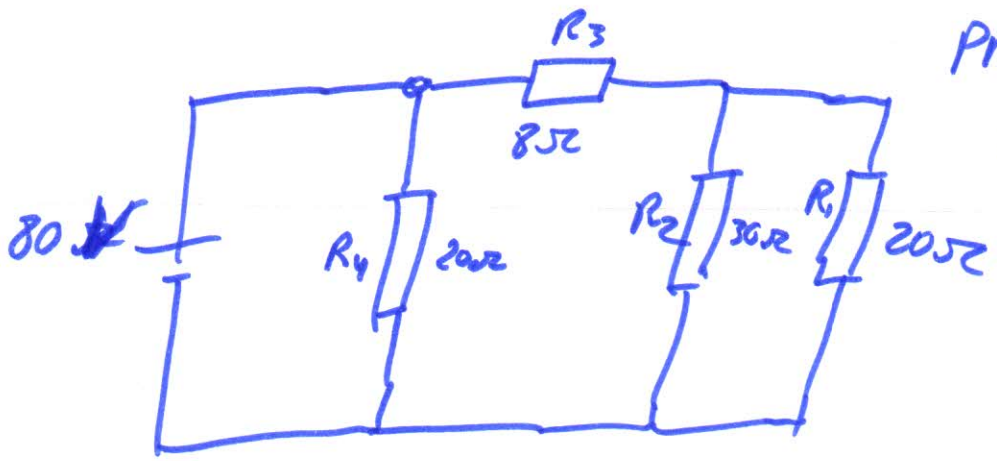

	Ω	V	I (A)	P (W)
\$R_1\$	20	48	2.4	115.2
\$R_2\$	30	48	1.6	76.8
\$R_3\$	8	32	4	128
\$R_4\$	20	80	4	320
\$R_{eq}\$	10	80	8	640

$$I = \frac{V}{R} = \frac{80}{10} = \underline{\underline{8A}}$$

$$V = R \cdot I \quad \parallel \quad I = \frac{V}{R}$$

$$P = V \cdot I$$

$$P = VI^2$$

$$P = \frac{V^2}{R}$$